

# A System for Video Conversion and Text Data Overlay

RAFIC BACHNAK

Texas A&M International University  
Dept. of Mathematical and Physical Sciences  
5201 University Blvd.  
Laredo, Texas 78045, USA  
[bachnak@ieee.org](mailto:bachnak@ieee.org)

RAMYA CHAKINARAPU, MARIO  
GARCIA, DULAL KAR

Texas A&M University-Corpus Christi  
Department of Computing Sciences  
6300 Ocean Drive  
Corpus Christi, Texas 78412, USA

*Abstract:* - This paper describes the design and development of a Video Conversion and Data Overlay (VCDO) prototype that takes in an analog National Television System Committee (NTSC) video signal generated by a video camera and data acquired by a microcontroller and display them in real-time on a digital panel. An 8051 microcontroller is used to acquire power dissipation by the display panel, room temperature, and camera zoom level. The paper describes the major hardware components and shows how they are interfaced into a functional prototype. Test data results are presented and discussed.

*Key-Words:* Overlaying Text Over Video, Data Conversion, Real-Time Video

## 1 Introduction

Text can be added to video sequences based on “layers.” The idea is to run two clips at the same time, one having the video and the other having the text. In order for the clip lying at the back to be visible, the text layer except for the actual text must be made transparent using transparency properties and background keying. Playing one clip on top of another is referred to as “superimposing,” often called matting or keying in television and film production [1]. Text in video frames can be classified as scene text and caption text. Scene text is text that occurs naturally in the 3-D scene being recorded and is distorted by perspective projection. Caption text comprises 2-D strings that are superimposed on to the video frame during the editing stage of production. Caption text is often referred to as overlay text, artificial text or superimposed text [2, 3]. Scene texts appear as part of the captured scene, like store signs, street tags, and shirt logos. Text overlays are superimposed on top of the scenes, and include video titles, news anchor names, and sport scores.

This paper describes a real-time device that overlays acquired data on a digital video signal. The project involves the design, development, and testing of several major components and interfacing them into a functional unit. The objective is to obtain useful physical parameters such as temperature value, power dissipated by a display, and zoom level of a camera and overlay them over a video signal in real time before sending them to the display. This device will enhance the capabilities of the Portable EVA Visual Inspection Tool (PEVIT) that is being developed at Johnson Space Center. This Non-destructive evaluation (NDE) inspection tool is for use during Extra Vehicular Activities (EVA) to allow visual on-orbit inspection of external Shuttle and International Space Station (ISS) structures in hard to reach areas. This capability becomes of increased importance as the orbiter fleet ages and the ISS grows in size. The overall system structure is shown in Figure 1. The black box that carries the NTSC video signal to the display device was configured to contain a video text overlay module to allow for text overlay, a controller to support the Liquid

Crystal Display (LCD) panel and a microcontroller to allow data acquisition and serial communication. The major components of the system are: a Charge Couple Device (CCD) camera with an analog NTSC video output, devices that perform text overlay and analog-to-digital conversion, and a LCD panel. Based on the system requirements, the initial components were CK3900 Analog NTSC video camera, the PD064VT4 TFT-LCD display panel, and the microMODUL-8051 Single Board Computer (SBC) controller board, the BOB-3 overlay module, and the SFD064VT4-ADV the LCD controller, which perfectly interfaces with the PD064VT4 display.

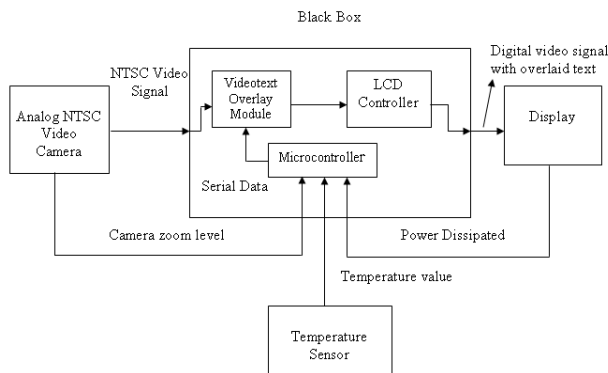


Fig. 1 Overall system block diagram

## 2 Major System Components

The following sections briefly describe these components.

### 2.1 Analog NTSC Video Camera

The camera used in the prototype is a NTSC Meiji Techno Analog CCD Color Camera CK3900N. The video signal can be obtained either by using the BNC connection or the S-Video connection as shown in Figure 2. Also pins 3 and 4 of the 9 pin Dsub simulates the Video out connection. This connection is utilized to minimize the wiring.

The main features of the camera follow.

- 450 TV lines of horizontal resolution
- TV Standard - NTSC or PAL
- NTSC: 525 lines, 768 x 494 @ 30 fps

- Super sensitive 1/2" sensor EXview HAD CCD
- Based on latest Digital Signal Processing (DSP)
- Composite VBS and Y/C video output
- S/N ratio >50dB
- Employs 9 pin Dsub connector at camera rear panel for single cable connection

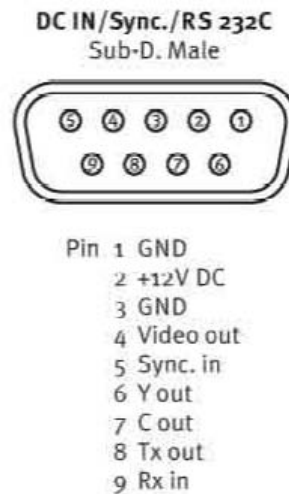


Fig. 2 Pin out of 9 pin Dsub

### 2.2 TFT LCD Panel

Thin-Film Transistor LCD (TFT-LCD) products have the advantage of being slim and lightweight with low radiation and low energy consumption. TFT-LCD display from Prime View Displays bearing a product number 'PD064VT4' was selected for this application. It operates in transmissive mode and hence needs a backlight. Features of the display follow.

- High contrast ratio: Contrast ratio is the ratio of the blackest black and the whitest white a TFT can display. The higher the contrast ratio, the better the image. The PD064VT4 offers a high contrast ratio of 400:1.
- Brightness: It is desired that the PEVIT display has a high brightness value. Brightness value of PD064VT4 is 400.
- Interface: TTL
- Operating temperature range -20°F to 70°F

### 2.3 Video Text Overlay Module

BOB-3 is designed in 30-pin SIMM (Single in-line Memory Module) form with supply voltage range of +5VDC  $\pm 5\%$  or +8~15V at 70mA typical. Factors considered in the selection of the BOB-3 are as follows:

- Data transmission path is asynchronous serial which is compatible with 8051 microcontroller.
- Supports varied baud rates of 1200, 2400, 4800, 9600, 19.2K, 38.4K, 76.8K, and 153.6K bits/sec. 8051 (Infineon C504) can be programmed to have baud rate of 2400 with 0.16% error.
- Serial communication parameters are 8 data bits, no parity, and one stop bit. The exact same parameters can be supplied from 8051 using one of its serial modes.
- Connects directly to the UART TXD/RXD pins of most microcontrollers
- Video environment is RS-170A (NTSC) composite base band.

### 2.4 LCD Controller Kit

A converter that allows successful signal transmission between analog and digital components is needed to convert the NTSC signal to digital. A LCD Controller board that interfaces the NTSC video signal with the PD064VT4 TFT LCD is needed. This controller should also have On-Screen Display (OSD) support. In other words the board has both the analog-to-digital converter (ADC) unit and an OSD unit integrated into a single board. Desired features of the controller follow.

- Video Input Signal: NTSC
- Interface Panel type: PD064VT TFT LCD
- Backlight inverter board included
- Controller to convert analog signals to digital
- OSD capabilities

The SFD064VT4, from AZ Displays, was identified as the interface board for PD064VT4 display panel.

### 2.5 The 8051 Microcontroller

The 8051 microcontroller development board, the microMODUL-8051 SBC from PHYTEC, is used in this project. Figure 3 shows a schematic of the board, which has the following features.

- On-board Flash-programming
- Requires a single power supply of 5V, typ. <200mA
- All ports and applicable logic signals extend to pin headers at the edges of the circuit board
- Controller signals and ports extend to standard-width (2.54 mm.) pins aligning board edges, allowing the board to be plugged into any target application like a “big chip” [4].

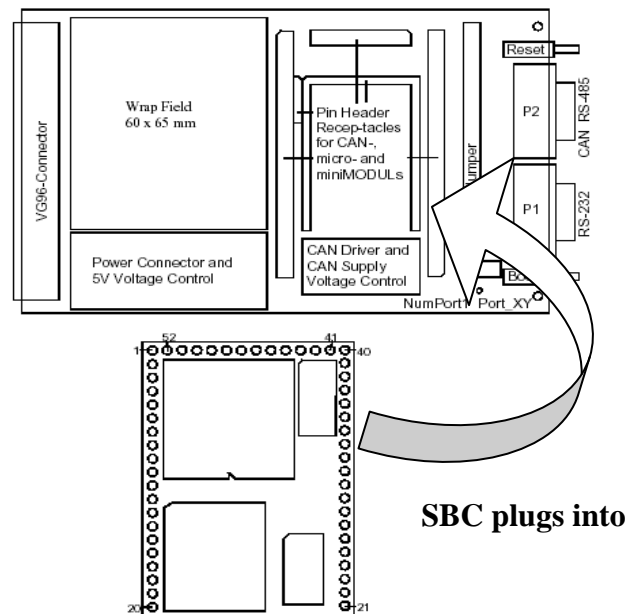


Fig. 3. The 8051 Development board

### 3 Data Acquisition

This section presents the mechanisms used to measure the parameters of interest; temperature, zoom level, and power dissipation. It also shows the interfacing of these components.

In order to capture any physical quantity for display, it has to be converted to digital data. This process involves two stages. In first stage, the physical quantity has to be converted to

electrical signal. In second stage an Analog-to-Digital converter is used to convert the electrical signal to a digital value. Figure 4 illustrates this process.

Analog quantities have to be converted to voltage before being sent to the 8051 ADC. And if the analog voltage range is lower than the range discernable by 8051 which is 0-5V, signal amplification (Signal Conditioning) might be necessary.

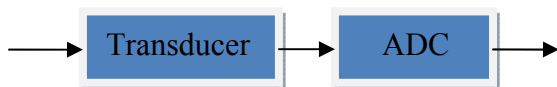


Fig. 4. Data acquisition process

### 3.1 Capturing Room Temperature

The LM34, a Fahrenheit temperature sensor manufactured by National Semiconductors, is used to capture the temperature value. LM34 series are widely used precision integrated-circuit temperature sensors. The LM34 is a voltage mode sensor whose output voltage is linearly proportional to the Fahrenheit temperature. It outputs 10 mV/°F. It is rated to operate over a  $-50^{\circ}\text{F}$  to  $+300^{\circ}\text{F}$  temperature range, which is a full span of  $350^{\circ}\text{F}$ . Moreover, LM34's low output impedance, linear output, and precise inherent calibration make interfacing to readout or control circuitry especially easy [5].

As the LM34 measures temperatures in the range of  $-50^{\circ}\text{F}$  to  $+300^{\circ}\text{F}$ , the corresponding voltages that are read from LM34 fall in the range -0.5V to 3.0V. But the 8051 can accept analog voltages in the range 0-5V and produces a 10-bit digital value. In order to make better utilization of 10-bit resolution provided by on-board ADC and to avoid a range of voltages being considered noise, the voltage signal ranging from 0.5V to 3.0V has been amplified to match the 8051 input range of 0V-5V. The voltage signal produced by the sensor is carried to the 8051 SBC via three stages; High-Impedance buffer stage, Gain stage and Inverting stage as shown in Figure 5. In the first stage the LM741 acts as a unity gain buffer amplifier otherwise called a voltage follower. A

voltage follower circuit makes a copy of the input voltage at the output without drawing any current from wherever the input voltage terminal is attached. It is necessary to have a high-impedance buffer stage between LM34 and gain stage to avoid loading the LM34 sensor as it would affect the voltage produced by sensor and thus the voltage measurement.

The second stage includes a basic inverting amplifier with an offset adjustment at the non-inverting input terminal of the LM741. The LM741 reads the voltage output of the first stage which indicates the temperature on a scale of 10mV/°F. Since the input voltage readings include negative voltages, it is necessary to offset the input voltage by 0.5V to obtain positive readings. Offset adjustment will give the readings in the range 0 to 3.5V. The 143K resistor in the feedback loop and the input resistance, a 100K Potentiometer (POT), are responsible for amplifying the signal to fall in the range 0-5V. Usage of a POT for the input resistor makes it possible to obtain variable gain.

Since the amplifier used in the second stage is an inverting amplifier, an additional stage is required to invert the output voltage. The third stage acts as an inverting stage to convert the negative signals to positive with a negligible gain. This temperature sensing circuit operates with an error of  $\pm 1$ .

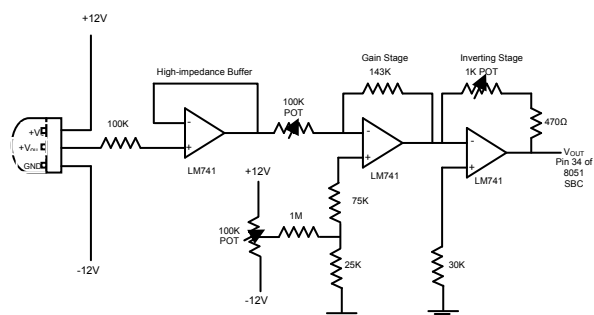


Fig. 5 Circuit for capturing temperature

### 3.2 Capturing Camera Zoom Level

Changing the focal length of the camera results in two important effects that are immediately obvious: lens' angle of view and its magnifying power. Angle of view refers to how much of a

scene the lens covers and magnification is inversely related to the lens' angle of view. Increasing the focal length, called zoom in, results in narrowing the angle of view and hence magnifying the objects in scene making them appear larger than they actually are. Conversely, decreasing the focal length (zooming out) results in widening the angle of view thus covering wide sweep of the scene and at the same time reducing the objects in the scene to fit into the image.

From the above explanation it is obvious that being able to capture the angle of view would allow computing the focal length. And converting the captured value to corresponding voltages is necessary to be able to feed the 8051 analog port. The idea behind developing the unit to capture the zoom value is to use a potentiometer having a movable wiper representing a transducer. The potentiometer is mechanically coupled to the zoom lens mechanism for generating a voltage signal representative of the viewing angle of zoom lens. The potentiometer is placed right below the lens as can be seen in Figure 6, in a way such that rotating the lens results in the movement of the potentiometer wiper producing varied voltage signal values.

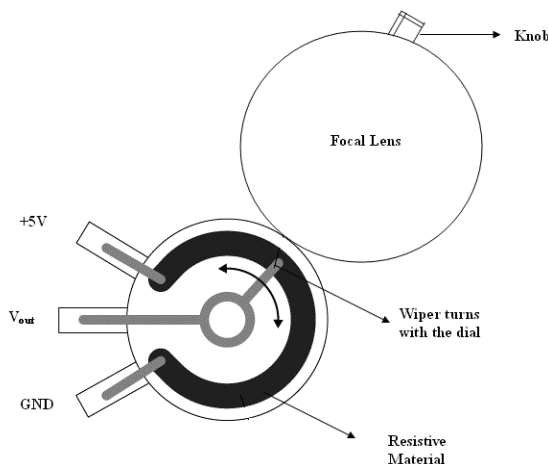


Fig. 6 Mechanism for capturing zoom level

In general, an analog level of 0% (0V) indicates that the lens is at its wide shot position and an analog level of 100% (4.3V) indicates that the

lens is at its tight shot position. Signal conditioning was not employed in developing this circuit as the obtained voltages lie in the range 0 - 4.3V which is close to the 0-5V analog input range of 8051. A formula to compute the zoom value or focal length is formulated based on the linear relation the voltage holds with the lens' angle of view. The unit operates with an error of +/- 0.2.

### 3.3 Capturing Power Dissipation

In order to calculate the power dissipated by the display panel and its accompanying components (LCD controller kit), a very small resistor of known value is placed in series with the display system. Capturing the voltage drop across this resistor helps determine the current flowing through the display. Since the supply voltage is constant and the amount of current flowing in the resistor and the display are always the same, it is enough to calculate the current flowing into the display to determine the total power dissipated.

The LM741, an operational amplifier manufactured by national Semiconductors, devices, is used as shown in Figure 7. The LM 741 in the first stage acts as a differential amplifier. The differential amplifier measures the difference between two input signals (-) and (+). The input signal at the inverting input terminal is the actual voltage supplied i.e., +12V and the input at non-inverting input terminal is the supplied voltage less the voltage dropped across the  $2\Omega$  resistor. As the variation in the current flowing through the display unit is very minute, in the range  $\pm 0.1$  or  $\pm 0.2$ , the voltage measured across the  $2\Omega$  resistor lies in the range -1.5V to -1.7V. The negative voltage output at this stage is due to the higher voltage input at the inverting input terminal. This leads to a second amplification stage that provides the necessary gain to match the output voltage range to the analog input range of the 8051 and also results in positive voltages.

The LM741 in the second stage is used to attain a variable gain and to offset the negative input voltages. This stage is similar to the second stage of the temperature capturing unit. This circuit also uses two capacitors each at

output points of two stages in order to slow down the response time. An LED is also attached to the output voltage point to illustrate the change in the amount of power dissipated at different lighting conditions.

The output produced by the developed unit is the amplified value of the voltage dropped across the  $2\Omega$  resistor. The circuit has a gain of 4.6 and a negative offset voltage of 1.42V. Therefore the actual voltage drop across the  $2\Omega$  resistor is obtained by dividing the voltage read less the offset voltage with the gain factor. In order to calculate the power ( $P = V * I$ ) dissipated by the display unit it is necessary to know the voltage (V) applied and the amount of current (I) flowing through the display. As the  $2\Omega$  resistor is in series with the display unit, the current flowing through the resistor is the same as the current flowing through the display unit. Amount of current flowing across resistor is calculated using Ohm's law ( $V = I * R$ ) since the values of V and R are known ( $V = 12V$  and  $R = 2\Omega$ ).

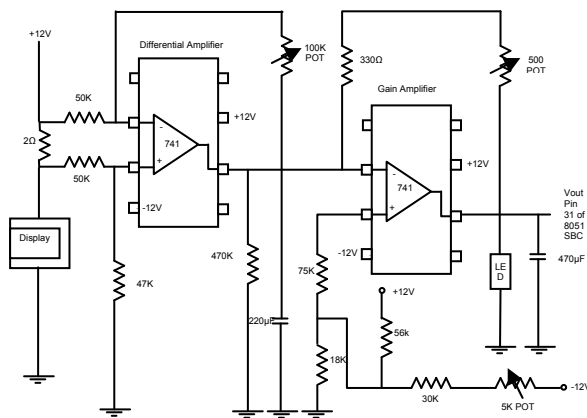


Fig. 7 Circuit for measuring power

### 3.4 Interfacing the Components

Hooking up the camera with BOB-3 was through the video out connection, pin 4 of the 9 pin Dsub connector, available on the back end of the camera and video in (pin 30) on BOB-3. With this interface the system gets its first input, the NTSC analog color video signal. Next, connecting the BOB-3 with 8051 was based on synchronizing the baud rate necessary for

establishing communication between the two components. Nearest baud rate of the 8051 (Infineon C504-L) microcontroller is programmed to match the 2400 baud rate range supported by the BOB-3, with an error rate of 0.16%. This error rate is acceptable as the communication is always possible as long as the error rate is less than 1%. The 8051 is programmed for 2400 baud rate while the BOB-3 is hard coded for 2400 baud rate making very few changes in its basic hook up as shown in Figure 8.

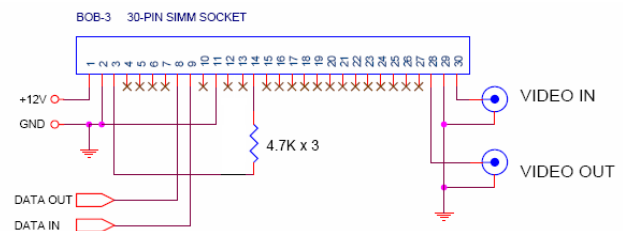


Fig. 8 Hook up for 2400 baud rate

The composite video out from pin 28 of BOB-3 which is an NTSC analog video signal with data parameters superimposed is carried to the PD064VT4 digital display via the SFD064VT4 – ADV boards. i.e., video signal from BOB-3 is supplied to the controller/driver board of the SFD064VT4 kit, at connection labeled CN9 in order to convert the analog video signal to digital video signal. The digital signal from driver board is carried to the display panel via a cable connected between CN2 of driver board and CN2 of Display panel. The inverter board is connected to display panel at connection CN1 in order to supply the back light necessary to light up the display. The Key board is connected to SFD064VT4 controller board (connection from CN1 of keyboard to CN3 of driver board) that allows controlling On Screen Display such as setting display parameters (contrast, brightness, sharpness, volume etc). Figure 9 shows a prototype of the system.

### 4 Programming

Programming the system was accomplished in C++ and assembly using  $\mu$ Vision3, an



Integrated Development Environment (IDE) that helps develop embedded applications [6-9]. FlashTools98 is a software program used to interact with the flash EEPROM located on the microcontroller module.



Fig. 9 Final system

$\mu$ Vision3 is an IDE (Integrated Development Environment) that helps develop embedded applications quickly and successfully. It integrates all tools including the C compiler, macro assembler, linker/locator, and HEX file generator. It is a Windows-based software development platform that encapsulates a project manager, make facility, tool configuration, editor and a powerful debugger. The target selected from the device database for this application is 'Infineon C504-L'. This is a C500 series CMOS controller with 8 ADCs, 32 I/O lines, 4 Timers/Counters, 12 Interrupts/2 priority levels and 512 bytes on-chip RAM that is compatible to standard 8051.

FlashTools98 is a software program used to interact with the flash EEPROM located on the microcontroller module. The flash device on board already has the necessary firmware needed to interact with FlashTools98 application running on the host PC. This software allows the user to download an application onto the microcontroller flash memory. FlashTools98 provides a serial interface to allow serial communication between PC and 8051 development board. The serial interface allows the user to select baud rate and serial port for communication. Serial port and baud rate used are COM1 and 9600

respectively.

#### 4.1 Programming the Controller

The 8051 is programmed for data acquisition and serial communication. The usual method of sending analog inputs to a microcontroller is to use an analog-to-digital converter. Analog-to-digital converter accepts an analog input voltage and converts it to a digital value that can be read by a microcontroller. However, 8051 SBC has an analog port to allow accepting analog inputs, an ADC to convert analog inputs to digital and also a serial interface that allows for serial data transmission. Most of the registers present in 8051 model have a specific function and hence are often referred to as Special Function Registers (SFR). There are a total of eleven SFRs present in 8051. The two 16-bit timers present can be used to generate time delay. These favorable features promote the use of 8051 SBC for this project.

#### 4.2 Analog-to-Digital Conversion

The three parameters, temperature, camera zoom, and the amount of power dissipated by the display, are analog quantities. Four pins of port3 (P3.2, P3.4, P3.5, P3.5) and four pins of port1 (P1.0, P1.1, P1.2, P1.3) form the analog port of 8051. These pins are aliased as AN0, ....., AN7 when acting as an analog port. As the system developed has only three analog inputs, three pins from port 3 have been selected as the input points. Setting these pins makes them act as analog pins. The input to these pins has to be voltages falling in range 0-5V.

Programming the on-chip analog-to-digital converter involves many special function registers namely ADCON0, ADCON1, ADDATH, ADDATL, SYSCON AND P3ANA. Bits 0, 1 and 2 of either ADCON0 or ADCON1 are used to determine the analog pin selection. Analog channel selection is internally carried out by a 3x8 multiplexer. The bits 0, 1 and 2 of ADCON1 or ADCON0 act as control pins to the MUX. Depending on the value of the control inputs MUX selects one of the 8 analog port pins. Register ADCON1 is also used to select the A/D converter clock pre-scaler ratio. BSY bit of ADCON0 register enables to keep

track of the analog-to-digital conversion process. P3ANA register controls the analog port pins present on port3. RMAP bit of SYSCON register provides access to P3ANA register. On-chip ADC has a resolution of 10 bits resulting in 1024 different digital values ranging from 0 - 1023. This 10-bit result of analog-to-digital conversion process is stored at ADDATH and ADDATL registers.

In order to display the value of a parameter, it has to be converted back to analog equivalent value to be human perceivable. Step size (resolution) which is the smallest change that can be discerned by an ADC has been an important parameter used to recalculate the analog value back from the digital value obtained. Step size for a voltage range of 0-5V is  $5/1024 = 4.89\text{mV}$ . i.e., change in input analog voltage should be at least 4.89mV (when  $V_{in}$  0-5V) for the change to be recognized by an ADC. That way ADC will be able to produce a value nearby 5 in 1024 steps. ( $1024*4.89 = 5V$  approx.)

### 4.3 Serial Communication

The main goal of this step is to establish serial communication between 8051 and BOB-3 module in order to send the digital data obtained serially through the on-chip UART (Universal Asynchronous Receiver and Transmitter). The three special function registers namely SBUF, SCON, PCON grouped as Serial Data Registers are of particular interest in this phase. The 8051 has a serial data communication circuit that uses register SBUF to hold data. Register SCON controls data communication, register PCON controls data rates, and pins RXD (P3.0) and TXD (P3.1) connect to the serial data network. SCON register is set to a value representing serial mode that uses 8 data bits and 1 stop bit matching the communication mode of BOB-3. Serial data communication circuit, the on-chip UART, can send data serially one byte at a time using SBUF. After the last bit of each byte has been transferred a serial transmit interrupt flag is set, indicating the circuit is ready for another transmission. This shows that each data byte transfer requires a particular amount of time. Hence, it is necessary to allow that time

between each transfer generating some time delay for every transfer.

The 8051 has two 16-bit timers. The delay required by serial communication can be achieved using these timers. The maximum increments a 16-bit counter can produce is  $2^{16}$  i.e., 65,535 increments, if the timer starts at 0. The timer increments for every 12 oscillator cycles. Crystal oscillator of the SBC used is a 12MHz crystal that oscillates 12,000,000 times a second. Hence for the timer to reach a value of 65535 it takes 12 times 65535 oscillations. And the time required for  $12*65535$  oscillations is 65.535 msec. Therefore the maximum delay a timer can produce starting at 0 is 65.535 msec. The delay routine has been programmed in Assembly. For this particular module Assembly was preferred to C as creating a Delay function in C would make the delay dependent on optimizer settings, compiler version and the memory model. Change being a constant thing in software world, new versions of C would naturally affect the functioning of this module. Purpose of the delay module is to stop the execution of the program for a specific time period. Therefore, change in the output of this module might produce unexpected results. So, to make the code 'future safe' the module had to be programmed in assembler.

## 5 Testing of the Prototype

The prototype was tested to examine its performance. In order to test for extreme conditions the LM34 sensor was exposed to liquid nitrogen to sense the negative temperatures below  $-50^{\circ}\text{F}$ , compressed air (freezer spray) to sense lower temperatures starting from  $0^{\circ}\text{F}$  and has been heated with the soldering iron to sense the temperatures ranging from room temperature to its maximum readable limit of  $300^{\circ}\text{F}$ . Table 1 illustrates the experimental results obtained when tested under different temperature conditions. The error is calculated as follows:  $\text{Error} = (T_t - T_e)$ .

Testing the zoom capture unit was quite easy as the lens is marked around the circumference of the zoom adjusting knob indicating the focal length.



Table 1 Temperature test results

| Exp. | V (V) | T <sub>i</sub> (°F) | Te (°F) | Error |
|------|-------|---------------------|---------|-------|
| 1    | 3     | 300                 | 299     | 1     |
| 2    | 0.75  | 75                  | 74.75   | 0.3   |
| 3    | -0.04 | - 4                 | -3.17   | -0.83 |
| 4    | -0.50 | -50                 | -49.6   | 0.4   |

Using the marked focal length values as test points the obtained zoom values were compared to test the accuracy of the results. Table 2 illustrates the experimental results obtained when tested for different focal length settings. The error is calculated as follows: Error = ( Z<sub>t</sub> - Ze).

Table 2 Zoom level test results

| Exp. | V (V) | Z <sub>t</sub> (mm) | Ze (mm) | Error |
|------|-------|---------------------|---------|-------|
| 1    | 4.30  | 8.5                 | 8.52    | -0.02 |
| 2    | 1.8   | 21                  | 21.01   | -0.01 |
| 3    | 0.9   | 33                  | 33.01   | -0.01 |
| 4    | 0     | 51                  | 50.90   | 0.1   |

Capturing power dissipation was tested under different lighting conditions to observe the variations in the amount of power utilized. Maximum power consumption of the display unit as per the datasheets is 8.4W. When the unit was tested under normal conditions it consumed 6.5 W approximately. The power consumption was reduced to 1.85 W when tested in a darker atmosphere. Maximum power consumption of 8.39 W was observed by testing the unit by increasing the brightness. Table 3 demonstrates the different power consumption observed under different lighting conditions.

Table 3 Power dissipation test results

| Exp | V (V) | I (mA) | P <sub>t</sub> (W) | Pe (W) | Error |
|-----|-------|--------|--------------------|--------|-------|
| 1   | 12    | 700    | 8.40               | 8.39   | 0.1   |
| 2   | 12    | 625    | 7.5                | 7.43   | 0.9   |
| 3   | 12    | 550    | 6.60               | 6.50   | 1.5   |
| 4   | 12    | 400    | 4.8                | 4.7    | 1.5   |

P<sub>t</sub> in column 4 is the theoretical value of the power dissipated (product of V applied and I obtained) and Pe in column 5 is the experimental value of the power dissipated as observed on the text over video. The error is calculated as follows: Error = ( P<sub>t</sub> - Pe).

## 6 Conclusion

This paper describes the design and development of a prototype that allows overlaying text onto a digital video signal in real-time. An 8051 microcontroller is programmed to capture the parametric values, convert them to digital signals, then serially transmit the data to the overlay module. Test results shows that the system achieved the desired results.

## Acknowledgement

This project is partially supported by NASA award #NCC5-517, NSF-MII award #0330822NSF, and the NASA Administrator Fellowship Program.

## References:

- [1] A Digital Video Primer. Available from <http://www.adobe.fr/products/dvcoll/pdfs/dvprimer.pdf>
- [2] Ullas Gargi, Sameer Antani, Rangachar Kasturi. Indexing Text Events in Digital Video Databases. *IEEE CNF*, (Aug 1998) 916-918 vol.1.
- [3] R. Bachnak, R. Chakinarapu, M. Garcia, D. Kar, T. Nguen, Real-Time Acquisition and

Display of Data and Video,” Proceedings of the 7<sup>th</sup> Int. Conf. on Signal Processing, Computational Geometry, and Artificial Vision (ISCGAV '07), pp. 233-239, Vouliagmeni, Athens, Greece, August 24-26, 2007

- [4] C504 8-bit CMOS Microcontroller User's Manual 11.97, Seimens AG, Fürth Bislohe, Oct 1997
- [5] The 8051 Microcontroller, 3<sup>rd</sup> Edition, Kenneth Ayala, Thomson, Delmar Learning, 2004
- [6]  $\mu$ Vision3 User's Guide, Keil Elektronik GmbH and Keil Software, Inc, TX, 2004
- [7] The 8051 Microcontroller and Embedded System, Muhammad Ali Mazidi and Janice Gillispie Mazidi, Prentice Hall, New Jersey, Nov 1999
- [8] BOB-3 Video Text Overlay module Application Guide Version 3.4. Decade Engineering, OR, 2005
- [9] Embedded C, Michael J. Pont, Addison Wesley Professional, NY, April 2.